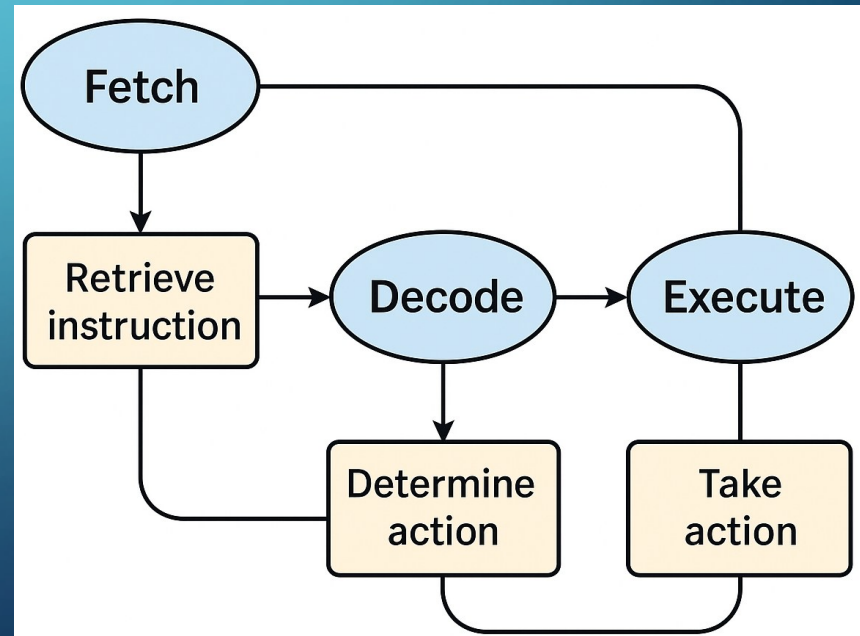


16-BIT RISC PROCESSOR DESIGN

- Design • Simulation
- Debug • Synthesis

OVERVIEW


- **Objective:** To Build a simple 16-bit RISC processor
- **Tools:** Verilog, Vivado
- **Pipeline:** Fetch, Decode, Execute, Write-Back



ARCHITECTURE

Components:

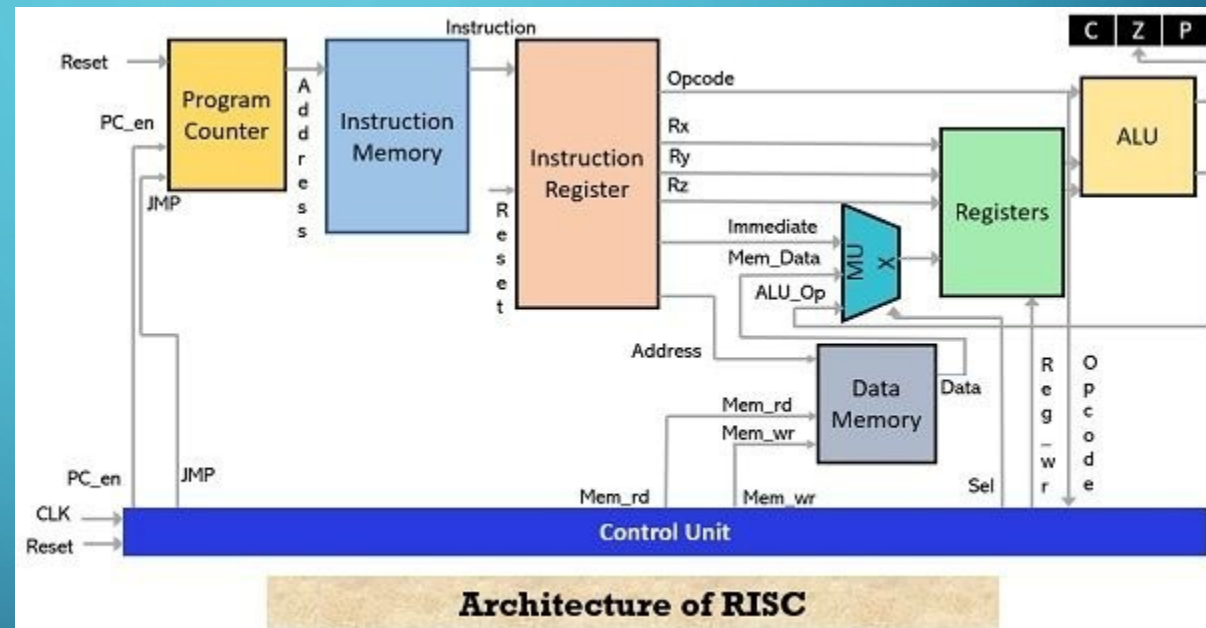- ALU, ALU Control Unit
- Register File
- Instruction Memory
- Data Memory
- Control Unit
- Data Path Unit
- Pipeline Stages



- 16-bit RISC ISA, single-cycle datapath
- Top-level: Risc_16_bit instantiates Control_Unit + Datapath_Unit
- Memory init via \$readmemb; simulation in Vivado

PIPELINE STAGES


- 1. Fetch – Instruction read
- 2. Decode – Register file read
- 3. Execute – ALU operations
- 4. Memory Access – Accesses data memory
- 5. Write-Back – Store results

1. FETCH

AINIP


2. DECODE

3. EXECUTE

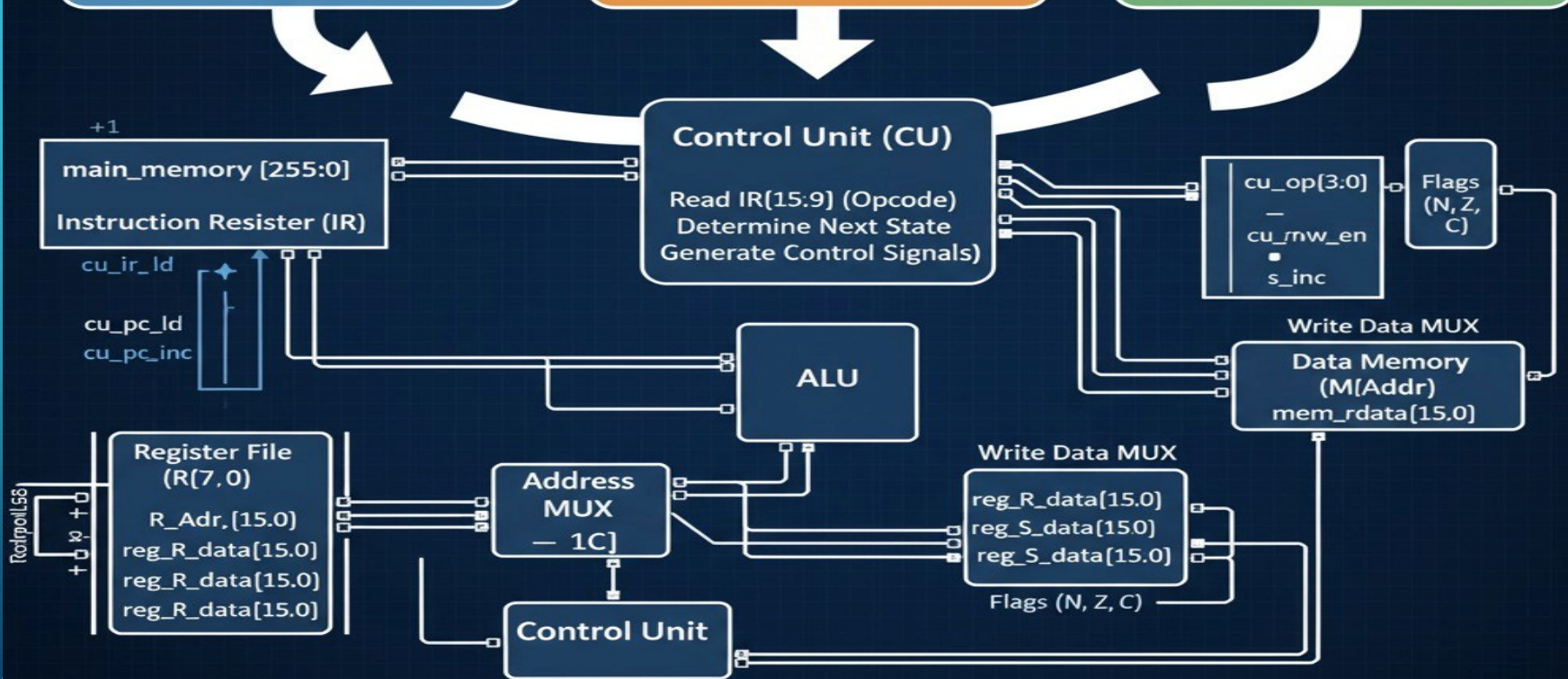

16-bit RISC Processor: FETCH-DECODE-EXECUTE Cycle

SCHEMATIC

 

INSTRUCTION SET

Operations:

- ADD, SUB, AND, OR, NOT
- Right Shift, Left Shift
- LOAD WORD, STORE WORD
- BRANCH instructions

The instruction set of the RISC processor:

A. Memory Access Instructions

1. Load word $LW \text{ } ws, \text{offset}(rs1) \text{ } ws := Mem16[rs1 + \text{offset}]$
2. Store Word: $SW \text{ } rs2, \text{offset}(rs1) \text{ } Mem16[rs1 + \text{offset}] = rs2$

B. Data Processing Instructions

1. Add: $\text{ADD } ws, rs1, rs2 \quad ws := rs1 + rs2$
2. Subtract: $\text{SUB } ws, rs1, rs2 \quad ws := rs1 - rs2$
3. Invert (1's complement): $\text{INV } ws, rs1 \quad ws := !rs1$
4. Logical Shift Left: $\text{LSL } ws, rs1, rs2 \quad ws := rs1 \ll rs2$
5. Logical Shift Right: $\text{LSR } ws, rs1, rs2 \quad ws := rs1 \gg rs2$
6. Bitwise AND: $\text{AND } ws, rs1, rs2 \quad ws := rs1 \cdot rs2$
7. Bitwise OR: $\text{OR } ws, rs1, rs2 \quad ws := rs1 \mid rs2$
8. Set on Less Than:
 $\text{SLT } ws, rs1, rs2 \quad ws := 1 \text{ if } rs1 < rs2; ws := 0 \text{ if } rs1 \geq rs2$

C. Control Flow Instructions

1. Branch on Equal: `BEQ rs1, rs2, offset`

Branch to $(PC + 2 + (offset \ll 1))$ when $rs1 = rs2$

2. Branch on Not Equal: `BNE rs1, rs2, offset`

Branch to $(PC + 2 + (offset \ll 1))$ when $rs1 \neq rs2$

3. Jump:

`JMP offset` Jump to $\{PC[15:13], (offset \ll 1)\}$

INSTRUCTION MEMORY

- The Instruction Memory stores the program that the processor executes. It outputs the 16-bit instruction corresponding to the current **Program Counter (PC)** value.

Key Features

- **16-bit wide ROM**
- Stores **up to 16 instructions** (memory[0] to memory[15])
- **Program loaded from external file** (test.prog)
- **Combinational access** → instruction available immediately when PC changes
- **Addressing uses PC bits [4:1]** to index instruction memory
- Implements the Fetch stage of the processor pipeline
- Allows easy program changes through the .prog file
- Provides a clean interface for the Control Unit and Datapath to decode and execute instructions
- Helps understand instruction flow inside a simple RISC CPU

INSTRUCTIONS USED (TEST.PROG)

- 0000_000_001_000000 // LW R0 <-Mem(R0 + 0)
- 0000_000_001_000001 // LW R1 <-Mem(R0 + 1)
- 0010_000_001_010_000 // ADD R2 <-R0 + R1
- 0110_000_001_010_000 // logical shift right R2 <-R0>>R1
- 0000_000_011_000010 // LW R3 <-Mem(R0 + 2)
- 0100_011_000_100_000 // NOT R4 <-~R3
- 1000_000_001_110_000 // OR R6 <-R0 | R1
- 1001_000_001_111_100 // Selecton less thanR7 <- (R0 < R1)

DATAPATH

Flow:

- PC → Instruction Memory
- Register Read
- ALU Execute
- Memory Access
- Write-Back to Register File

DATA MEMORY

- The Data Memory block stores and retrieves 16-bit data during program execution.
It supports both **read** and **write** operations and is used by load/store instructions in the RISC processor.

Key Features

- **8 × 16-bit memory array** (memory[0] to memory[7])
- **Synchronous write** on the rising edge of clock
- **Combinational read** when mem_read = 1
- **Address mapped using lower 3 bits** (mem_access_addr[2:0])
- **Memory contents initialized from external file** (test.data)
- **Live monitoring of memory values** using \$fmonitor for debug/logging

Generates control signals:

- ### Processor Control Unit Design:

[illegible]

ALU

```
`timescale 1ns / 1ps
```

```
module ALU(
```

```
    input [15:0] a,b, //src1 AND //src2
```

```
    input [2:0] alu_control, //function sel
```

```
    output reg [15:0] result, //result
```

```
    output zero, Negative, Parity );
```

```
always @(*)
```

```
begin
```

```
    case(alu_control)
```

```
        3'b000: result = a + b; // add
```

```
        3'b001: result = a - b; // sub
```

```
        3'b010: result = ~a;
```

```
        3'b011: result = a<<b;
```

```
        3'b100: result = a>>b;
```

```
        3'b101: result = a & b; // and
```

```
        3'b110: result = a | b; // or
```

```
        3'b111: begin if (a<b) result = 16'd1;
```

```
                    else result = 16'd0;
```

```
                    end
```

```
        default: result = a + b; // add
```

```
    endcase
```

```
end
```

```
assign zero = (result==16'd0) ? 1'b1: 1'b0;
```

```
assign Negative = result[15]; // MSB indicates  
sign
```

```
assign Parity = ^(result); // XOR of all bits →
```

```
odd parity = 1, even = 0
```

```
endmodule
```


ALU CONTROL UNIT

ALUOp	Opcode(hex)	ALUcnt	ALU Operation	Instruction
10	xxxx	000	ADD	LW,SW
01	xxxx	001	SUB	BEQ,BNE
00	0002	000	ADD	D-type: ADD
00	0003	001	SUB	D-type: SUB
00	0004	010	INVERT	D-type: INVERT
00	0005	011	LSL	D-type: LSL
00	0006	100	LSR	D-type: LSR
00	0007	101	AND	D-type: AND
00	0008	110	OR	D-type: OR
00	0009	111	SLT	D-type: SLT

ALU_CONTROL VERILOG CODE


```
`TIMESCALE 1NS / 1PS
MODULE ALU_CONTROL( ALU_CNT, ALUOP, OPCODE);
  OUTPUT REG[2:0] ALU_CNT;
  INPUT [1:0] ALUOP;
  INPUT [3:0] OPCODE;
  WIRE [5:0] ALUCONTROLIN;
  ASSIGN ALUCONTROLIN = {ALUOP,OPCODE};
  ALWAYS @(ALUCONTROLIN)
  CASEX (ALUCONTROLIN)
    6'B10XXXX: ALU_CNT=3'B000;
    6'B01XXXX: ALU_CNT=3'B001;
    6'B000010: ALU_CNT=3'B000;
    6'B000011: ALU_CNT=3'B001;
    6'B000100: ALU_CNT=3'B010;
    6'B000101: ALU_CNT=3'B011;
    6'B000110: ALU_CNT=3'B100;
    6'B000111: ALU_CNT=3'B101;
    6'B001000: ALU_CNT=3'B110;
    6'B001001: ALU_CNT=3'B111;
    DEFAULT: ALU_CNT=3'B000;
  ENDCASE
ENDMODULE
```


TESTBENCH

```
`timescale 1ns / 1ps
`include "Parameter.v"

module tb;
reg clk ;
wire [15:0] result;
initial
begin
    clk <=0;
    `simulation_time;
    $finish;
end
always
begin
    #5 clk = ~clk;
end
    Risc_16_bit uut(.clk(clk), .result(result),.z_flag(z_flag),.p_flag( p_flag));
endmodule
```


VIVADO WAVEFORM

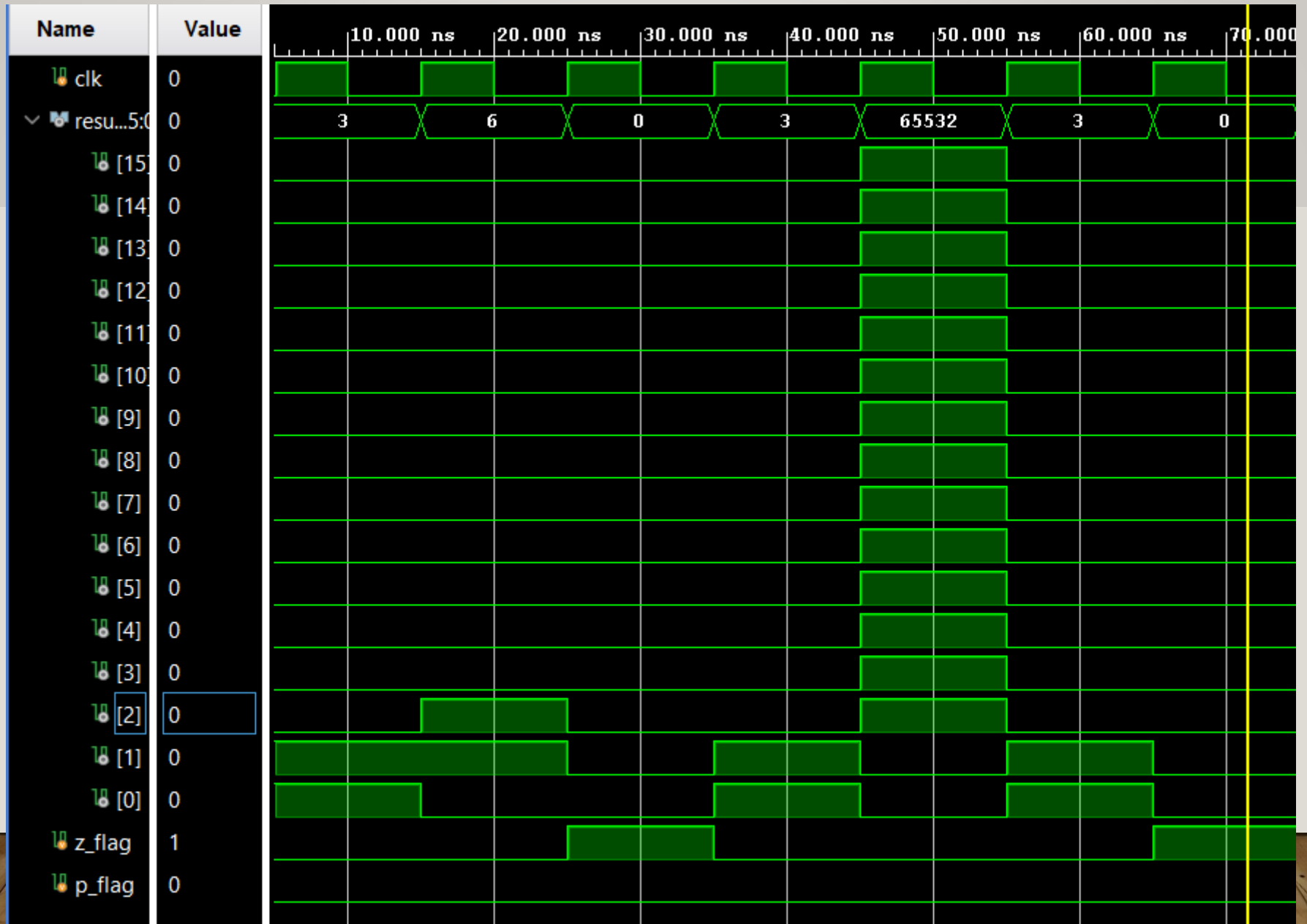

SYNTHESIS AND IMPLEMENTATION

Design Timing Summary

Setup

Worst Negative Slack (WNS): 0.176 ns
Total Negative Slack (TNS): 0.000 ns
Number of Failing Endpoints: 0
Total Number of Endpoints: 244


Hold

Worst Hold Slack (WHS): 0.376 ns
Total Hold Slack (THS): 0.000 ns
Number of Failing Endpoints: 0
Total Number of Endpoints: 244


Pulse Width

Worst Pulse Width Slack (WPWS): 3.750 ns
Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0
Total Number of Endpoints: 69

On-Chip Power

 

Dynamic: 0.054 W (43%)

 

Clocks: 0.001 W (1%)
Signals: 0.005 W (9%)
Logic: 0.003 W (6%)
I/O: 0.045 W (84%)

Device Static: 0.072 W (57%)

HAZARDS HANDLING

- Structural hazards avoided
- No data hazards due to simplified design
- Control hazards handled by PC update logic

OUTCOME

- Working 16-bit processor implemented
- Reinforced understanding of CPU architecture
- Hands-on experience with RTL, simulation & synthesis
- Foundation for advanced VLSI/CPU projects

REFERENCES

- Source: isroset.org
<https://share.google/KBrFRzuKuID7NFgif>
- M. Morris Mano

THANKYOU

SUBMITTED TO:

Dr Nitesh Kashyap

Assistant Professor (Grade-I)

ECE, NIT Jalandhar

SUBMITTED BY:

Sathwik 25204132

Aditya 25904138

Vishnu 25904150

M.Tech VLSI Design

1st Semester